

Department of Computer Engineering
Faculty of Engineering, University of Peradeniya

CO221 : Digital Design
Lab 6 - Prelab

-
- Each individual should have a written/printed pre-report.
 - No need to waste your time unnecessarily on neatness.
 - Write down the intermediate steps while you solve the problem.
 - If you need help put a post in the forum for CO221 in FEeLS rather than copying from someone else.
 - If you are caught copying you get 0 for the prelab and also the marks for the rest of the lab would be reduced by 50%.
-

1. Briefly explain why NAND and NOR gates are called universal gates. (One or two sentences would suffice)
2. Doing a design only using universal gates may sometimes complicate the circuit, but yet it is advantageous. State a such important advantage.
3. Show how all the other logic functions (NOT, AND, OR, NOR, XOR) can be implemented by **only using NAND** gates by drawing a logic circuit for each logic function.
4. Show how all the other logic functions (NOT, AND, OR, NAND, XOR) can be implemented by **only using NOR** gates by drawing a logic circuit for each logic function.
5. Implement the full adder circuit. The full adder has 3 inputs A , B , C_{in} where A , B are the input bits of the numbers and C_{in} is the carry in. There are 2 outputs S and C_{out} where S is the sum bit and C_{out} is the carryout.
 - a. Draw the truth table.
 - b. Draw the Karnaugh maps.
 - c. Derive the simplest Boolean equations.
 - d. Draw the logic circuit by using **2-input NOR gates** only.

6. Design a binary to BCD converter. Let the input be a 4-bit binary number ABCD. Let the output PQRS be the 4-bit BCD representation. Please note that input values only from 0-9 have BCD representations. For input values from 10-15 which are invalid, you should use don't cares.
- Draw the truth table.
 - Draw the Karnaugh maps.
 - Derive the simplest Boolean equations.
 - Draw the logic circuit by only using **2-input and/or 3-input NAND gates**.
7. Design a comparator circuit that compares the magnitude of two 2-bit numbers (AB and CD). It should have a 3-bit output PQR indicating $AB > CD$, $AB = CD$ and $AB < CD$ respectively.
- Draw the truth table.
 - Draw the Karnaugh maps.
 - Derive the Boolean equations that uses minimum number of gates.
 - Draw the logic circuit by only using **2-input and/or 3-input NAND gates**.