


Digital Design 3e, Morris Mano
Chapter 2 – Boolean Algebra and Logic Gates
Dr. Eng. Kamalanath Samarakoon

Overview

- Logic functions with 1's and 0's
 - Building digital circuitry
- Truth tables
- Logic symbols and waveforms
- Boolean algebra
- Properties of Boolean Algebra
 - Reducing functions
 - Transforming functions

Digital Systems


- Analysis problem:

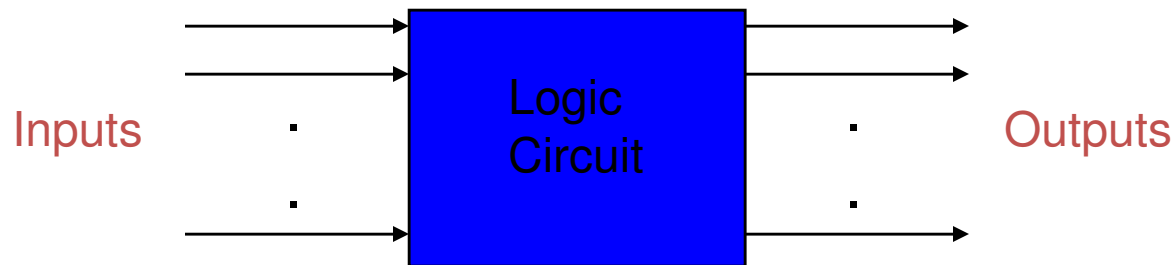


- Determine binary outputs for each combination of inputs
- Design problem: given a task, develop a circuit that accomplishes the task
 - Many possible implementation
 - Try to develop “best” circuit based on some criterion (size, power, performance, etc.)

Toll Booth Controller

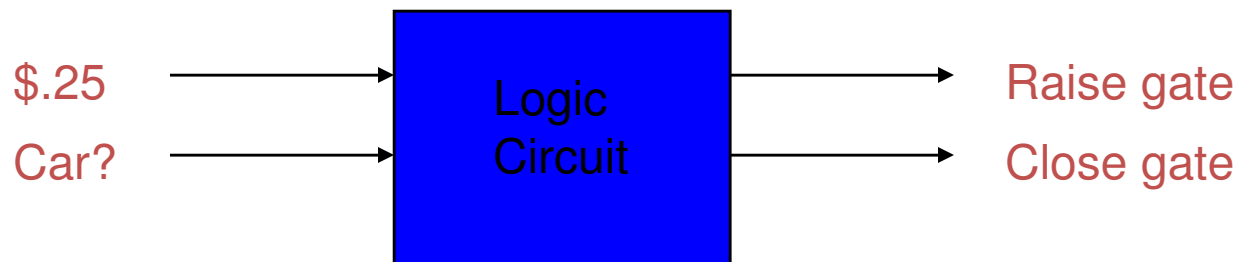- Consider the design of a toll booth controller
- Inputs: quarter, car sensor
- Outputs: gate lift signal, gate close signal



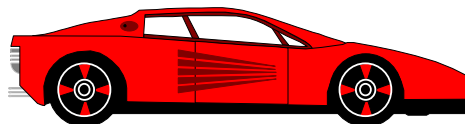- If driver pitches in quarter, raise gate.
- When car has cleared gate, close gate.



Describing Circuit Functionality: Inverter



Symbol

Truth Table

A	Y
N	Y
Y	N

Input

A	Y
F	T
T	F

Output

- Basic logic functions have symbols.
- The same functionality can be represented with truth tables.
 - Truth table completely specifies outputs for all input combinations.
- Why it is called truth table?
- The above circuit is an inverter.
 - An input of 0 is inverted to a 1.
 - An input of 1 is inverted to a 0.

A	Y
0	1
1	0

Positive logic and Negative Logic

- Positive logic
 - $0 = 0V$
 - $1 = 5V$
- Negative logic
 - $0 = 5V$
 - $1 = 0V$

The AND Gate




- This is an AND gate.
- So, if the two inputs signals are asserted (high) the output will also be asserted. Otherwise, the output will be deasserted (low).

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1


The OR Gate

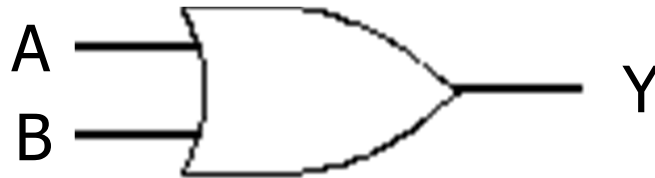

- This is an OR gate.
- So, if either of the two input signals are asserted, or both of them are, the output will be asserted.

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

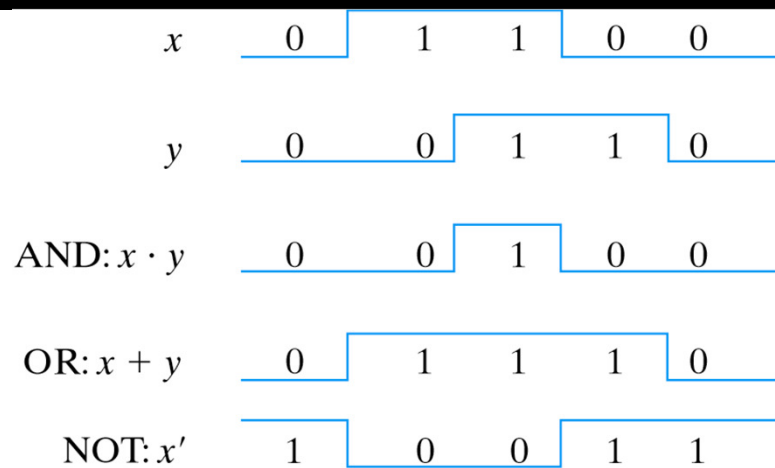Describing Circuit Functionality: Waveforms





AND Gate

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Fig. 1-5 Input-output signals for gates

- Waveforms provide another approach for representing functionality.
- Values are either high (logic 1) or low (logic 0).
- Can you create a truth table from the waveforms?

Consider three-input gates

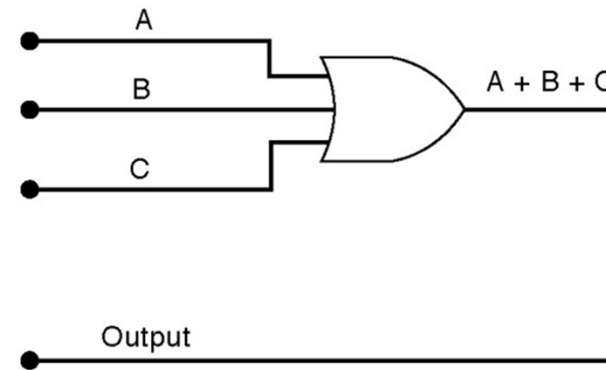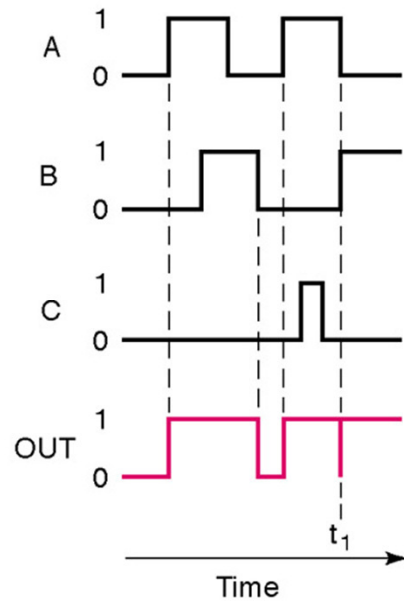


3 Input OR Gate

Circuit diagram of a 3-input OR gate. The inputs are labeled A, B, and C. The output is labeled $x = A + B + C$.

0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

Ordering Boolean Functions

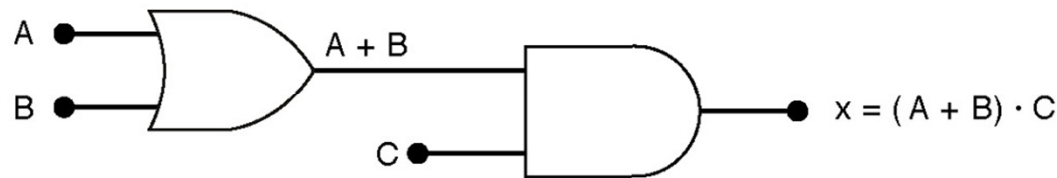- How to interpret $A \bullet B + C$?
 - Is it $A \bullet B$ ORed with C ?
 - Is it A ANDed with $B + C$?
- Order of precedence for Boolean algebra:
AND before OR.
- Note that parentheses are needed here :



Boolean Algebra

- A *Boolean algebra* is defined as a closed algebraic system containing a set K or two or more elements and the two operators, $.$ and $+$.
- Useful for identifying and *minimizing* circuit functionality
- Identity elements
 - $a + 0 = a$
 - $a . 1 = a$
- 0 is the identity element for the $+$ operation.
- 1 is the identity element for the $.$ operation.

Commutativity and Associativity of the Operators

- The Commutative Property:

For every a and b in K ,

$$- a + b = b + a$$

$$- a \cdot b = b \cdot a$$

- The Associative Property:

For every a , b , and c in K ,

$$- a + (b + c) = (a + b) + c$$

$$- a \cdot (b \cdot c) = (a \cdot b) \cdot c$$

Distributivity of the Operators and Complements

- The Distributive Property:

For every a , b , and c in K ,

$$- a + (b \cdot c) = (a + b) \cdot (a + c)$$

$$- a \cdot (b + c) = (a \cdot b) + (a \cdot c)$$

- The Existence of the Complement:

For every a in K there exists a unique element called a' (*complement of a*) such that,

$$- a + a' = 1$$

$$- a \cdot a' = 0$$

- To simplify notation, the \cdot operator is frequently omitted. When two elements are written next to each other, the AND (\cdot) operator is implied...

$$- a + b \cdot c = (a + b) \cdot (a + c)$$

$$- a + bc = (a + b)(a + c)$$

Duality

- The principle of *duality* is an important concept. This says that if an expression is valid in Boolean algebra, the dual of that expression is also valid.
- To form the dual of an expression, replace all + operators with . operators, all . operators with + operators, all ones with zeros, and all zeros with ones.
- Form the dual of the expression
$$a + (bc) = (a + b)(a + c)$$
- Following the replacement rules...
$$a(b + c) = ab + ac$$
- Take care not to alter the location of the parentheses if they are present.

Involution

- This theorem states:

$$(a')' = a$$

- Taking the double inverse of a value will give the initial value.

Absorption

- This theorem states:

$$a + ab = a$$

$$a(a+b) = a$$

- To prove the first half of this theorem:

$$a + ab = a \cdot 1 + ab$$

$$= a (1 + b)$$

$$= a (b + 1)$$

$$= a (1)$$

$$a + ab = a$$

DeMorgan's Theorem

- A key theorem in simplifying Boolean algebra expression is DeMorgan's Theorem. It states:

$$(a + b)' = a'b'$$

$$(ab)' = a' + b'$$

- Complement the expression $a(b + z(x + a'))$ and simplify.

$$\begin{aligned}(a(b+z(x + a')))' &= a' + (b + z(x + a'))' \\ &= a' + b'(z(x + a'))' \\ &= a' + b'(z' + (x + a'))' \\ &= a' + b'(z' + x'a'') \\ &= a' + b'(z' + x'a)\end{aligned}$$

Summary

- Basic logic functions can be made from AND, OR, and NOT (invert) functions
- The behavior of digital circuits can be represented with waveforms, truth tables, or symbols
- Primitive gates can be combined to form larger circuits
- Boolean algebra defines how binary variables can be combined
- Rules for associativity, commutativity, and distribution are similar to algebra
- DeMorgan's rules are important.
 - Will allow us to reduce circuit sizes.

Acknowledgement

- Dr. Swarnalatha Radakrshnan