

# DEVICES AND COMMUNICATION BUSES FOR DEVICES NETWORK–

## Lesson-7: Parallel Port Interfacing with Switches, Keypad and Rotatory encoder

## Port Interfacing — Parallel port outputs O0 to O7


- May be used as poll-lines— A line sends a logic state for sensing a present state of a key
- May be to switch on-off the LEDs
- May be to switch on the LEDs near the slots with photo-transistors at other end

## Port Interfacing— Parallel port inputs I0 to I7

- May be from a keypad controller for ASCII code of the pressed key
- From interface circuit of sense-lines for sensing key-state
- From phototransistors

# 1. Parallel Port Interfacing with Switches (at camera or automatic chocolate vending machine) or menu select keys
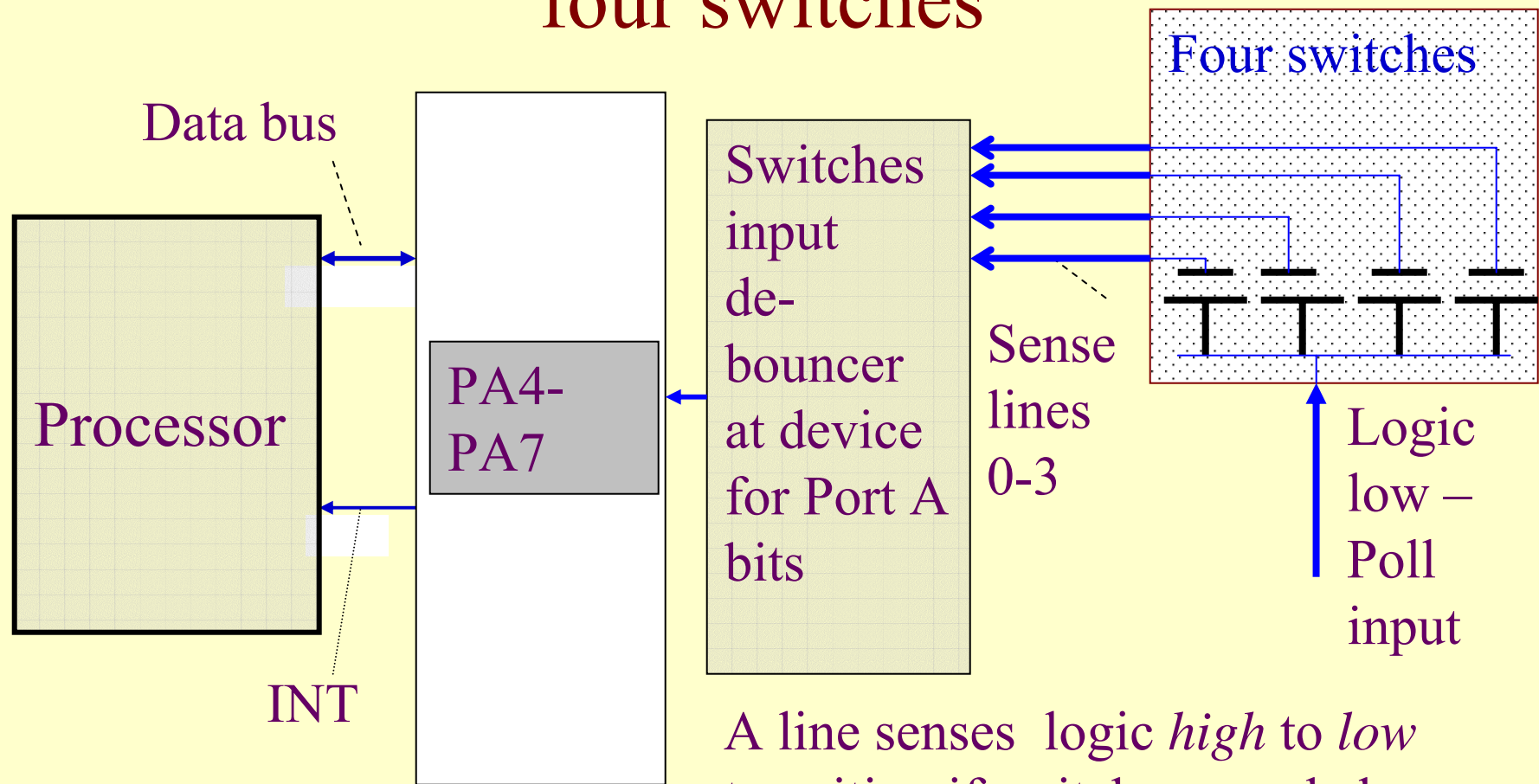
# Parallel port A with four-bit input from four switches



A line senses logic *high* to *low* transition if switch pressed else *high*

## 2. Parallel Port Interfacing with Keypad

# Keypad

- Physical lay out can be  $3 \times 5$  plus 1 or 16 in a one row
- 16 keys assumed to be divided in four columns and four rows for circuit design
- One column connects to one poll line
- One key in a row connects to one sense line

## 16-keys keypad and Four Menu keys


- Mobile smart phone has 16 keys and four menu select up, down, left, right keys
- A processing element– a keypad controlling-device (controller)




## A set of switches or keypad of 16 keys and four menu-select keys

- Assume that idle state logic state = 1.
- Four bits of an 8 bit input port A (A4-A7) for four menu select keys.
- 16 keys –arranged in four rows and four columns.
- Other four bits of A (A0-A3)–input from four common ends of four rows.
- Four bits of output port C (C0-C3)– output to four common ends of four columns.

# Keypad

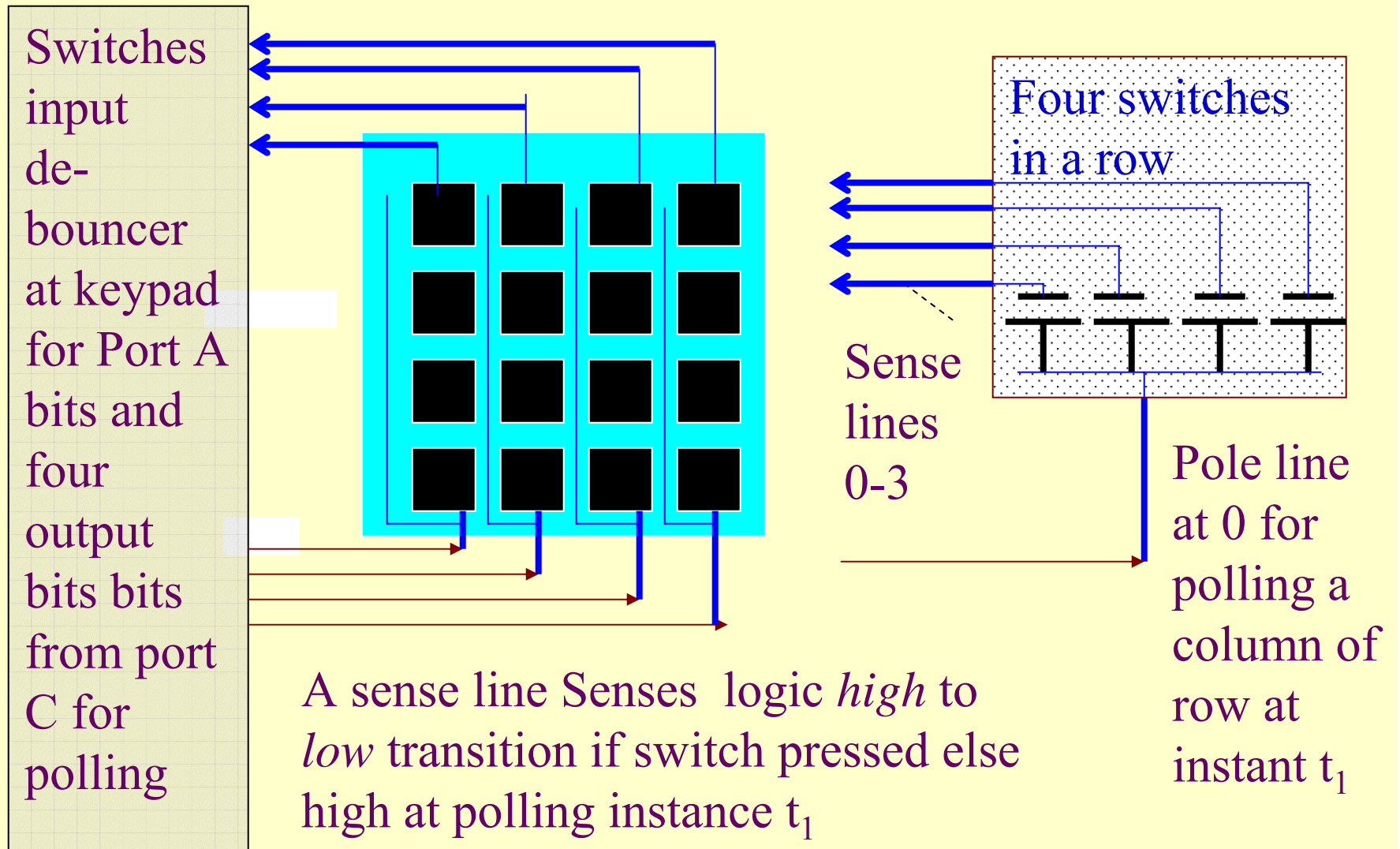
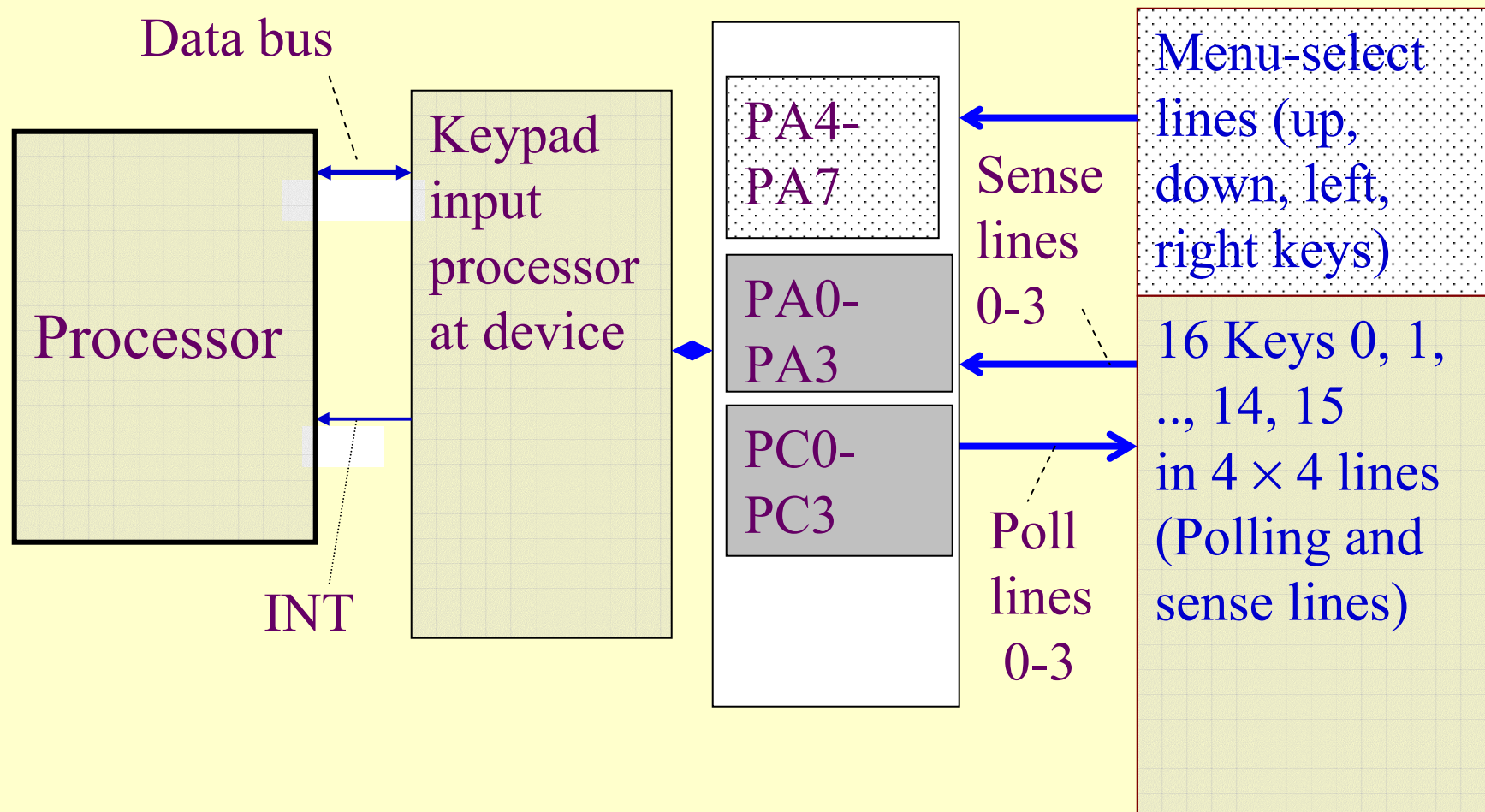
# Parallel input port A and four-bit output port C used for interfacing a set of 16 keys in keypad and four menu select keys



A processing element — keypad controller, as  
it is keypad specific.

## Processing element in the device

- Activates for polling output from port *C* ten times each second
- Sends  $C0-C3 = 0000$  and after a wait it reads  $D0-D7$  and  $A4-A7$
- Processes the bounces when a key is pressed. This takes care of bouncing effects.

## Processing element in the device

- Processing element computes the code of the pressed key and generates a status signal when a key is found pressed. From the bit pattern found at A0-A3, the processing element computes the 7-bit ASCII code of the pressed key at that instance and send output for the code through D0-D6. It also outputs  $D7 = 1$  if a key is found pressed else  $D7 = 0$ .

### 3. Parallel Port Interfacing with encoder

# Encoder

- A device, which measures the angular or linear position of a rotating or moving shaft
- Application in robots and industrial plants



# Rotatory angle encoder

- Multiple tracks on a rotating disk.
- Each track has half of the segments transparent and half opaque.

# Rotatory Encoder

- A has multi-slotted plate. A set of  $n$  infrared (IR) LED and phototransistor pairs generate  $n$ -bit input for a port.
- The encoder's each phototransistor interfaces to one parallel port bit

## Rotatory Encoder interfacing

- Seven inputs— Five track Rotatory encoder, one input is from PT at index slot, one input from phase detector circuit
- Six outputs to six LEDs


## Five tracks and one index slot

- One index slot is required to know the beginning of a revolution i.e. the position when shaft angle =  $0^\circ$
- Five tracks are required to find the present angular position of a shaft with resolution of  $360^\circ/2^5$
- Phase angle detection between adjacent tracks gives the direction of motion

## Interfacing of Six LED-Phototransistor Pairs and one phase detector circuit

- Five track Rotatory encoder has six LED-phototransistor (PT) pairs
- Five inputs are PTs from tracks and one input is from PT at index slot
- One input is from phase detector circuit, which finds phase angle between input from two PTs
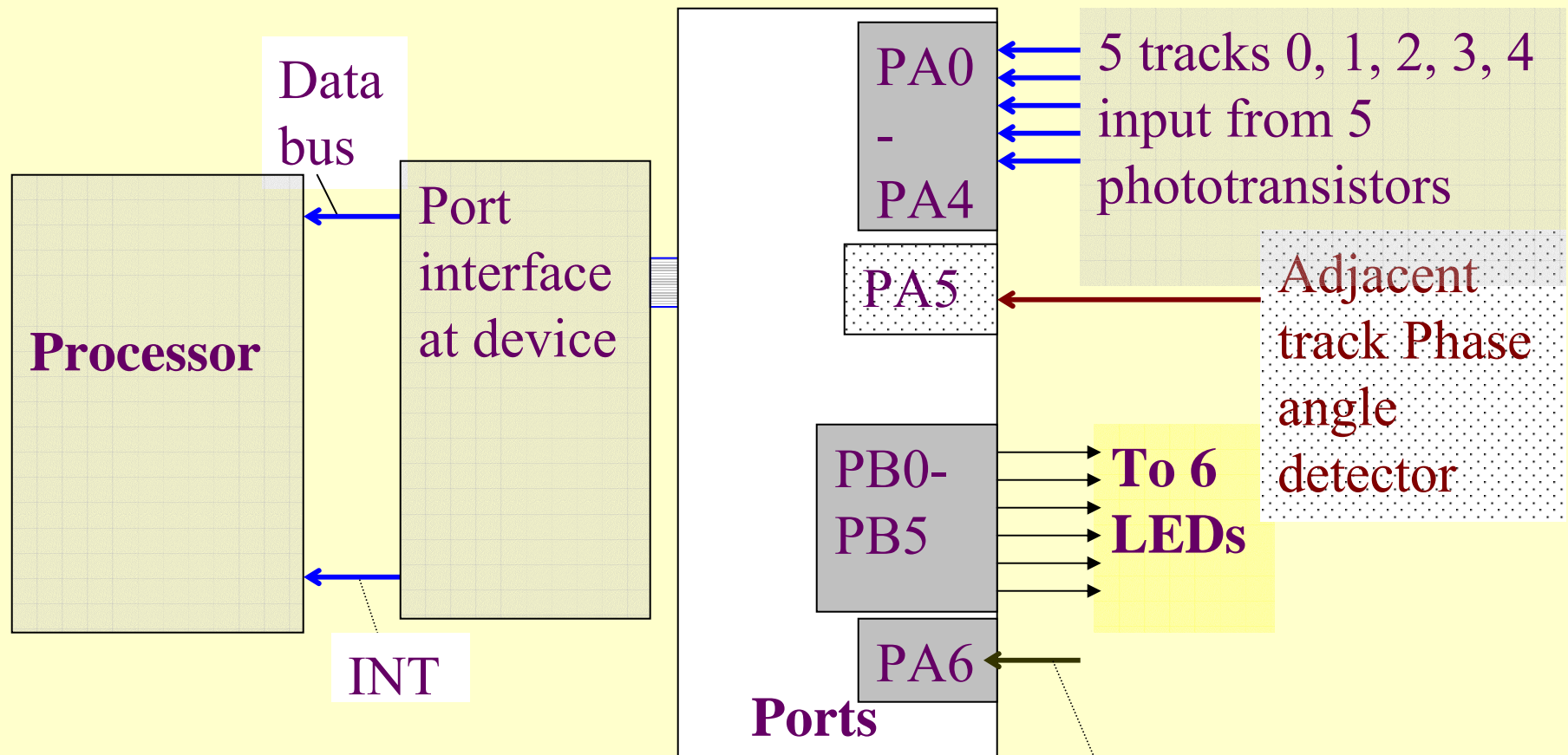
# Parallel input port A connected to an encoder circuit which sends the rotated or linear position of a moving shaft



**PA6 input from index slot phototransistor in the rotating plate**

# Summary

We learnt

- Parallel port input from switches – A poll line at logic 0 connects one end of a switch and other end of a switch, which is at 1 in released state, senses 0 when pressed.
- Four sense lines from four switches to four port pins
- Port bit sensed = 0 when switch pressed and = 1 when released



We learnt

- Each switch or key de-bouncing circuit
- Parallel port input from 16-key keypad
- Keys assumed to be divided in four columns and four rows
- Four poll lines at logic 0 outputs (from four port pins) connect four columns of switches
- Four sense lines from four switches in a row to four port pins

We learnt

- Parallel port input from four menu keys
- Rotatory Encoder
- Rotatory Encoder seven inputs— Five track Rotatory encoder, one input is from PT at index slot, one input from phase detector circuit
- Rotatory Encoder Six outputs to six LEDs

# End of Lesson 7 of Chapter 3