

# EE281 (Introduction to Electrical Engineering II) and EE285 (Electronics I)

## Bipolar Junction Transistor (BJT)

Dr. Melaka Senadeera  
Department of Electrical and Electronics Engineering  
University of Peradeniya  
Peradeniya



# Bipolar Junction Transistor (BJT)



- What is a Transistor?
- History
- Types
- Characteristics
- Applications




# What is a transistor ?

- Semiconductors: ability to change from conductor to insulator
- Can either allow current or prohibit current to flow
- Useful as a switch, but also as an amplifier
- Essential part of many technological advances
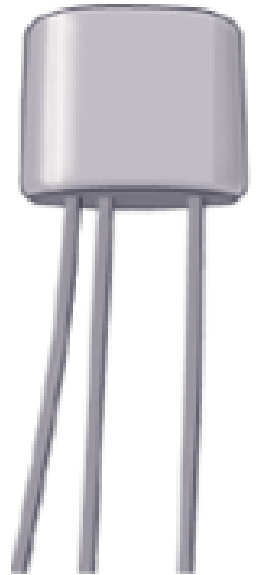
# What is a transistor ?




- Semiconductors: ability to change from conductor to insulator
- Can either allow current or prohibit current to flow
- Useful as a switch, but also as an amplifier
- Essential part of many technological advances



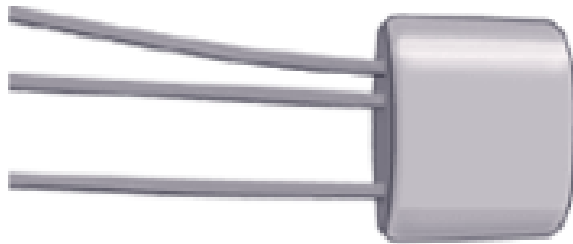
# The Transistor is Born



- Bell Labs (1947): Bardeen, Brattain, and Shockley
- Originally made of germanium
- Current transistors made of doped silicon




# How Transistors Work


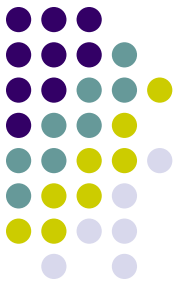


- Doping: adding small amounts of other elements to create additional protons or electrons
- P-Type: dopants lack a fourth valence electron (Boron, Aluminum)
- N-Type: dopants have an additional (5<sup>th</sup>) valence electron (Phosphorus, Arsenic)
- Importance: Current only flows from P to N


# Diodes and Bias

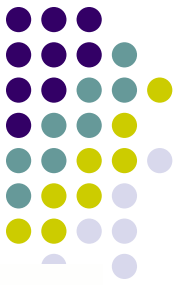

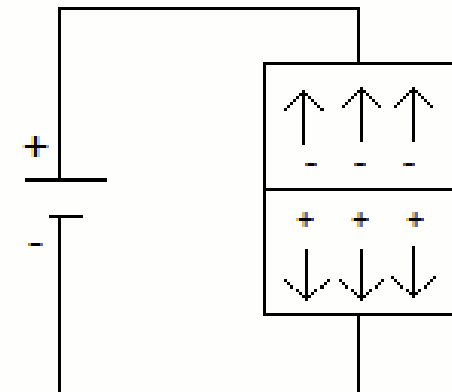
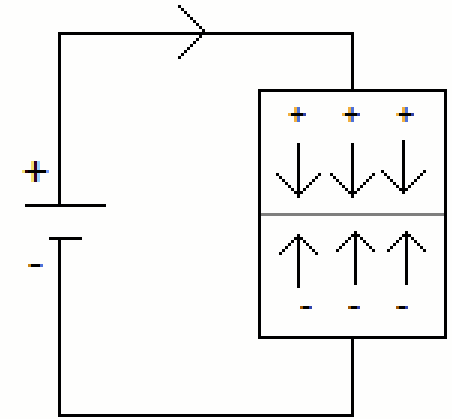
- Diode: simple P-N junction.
- Forward Bias: allows current to flow from P to N.
- Reverse Bias: no current allowed to flow from N to P.
- Breakdown Voltage: sufficient N to P voltage of a Zener Diode will allow for current to flow in this direction.



# Bipolar Junction Transistor (BJT)

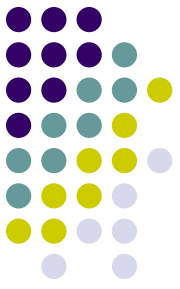

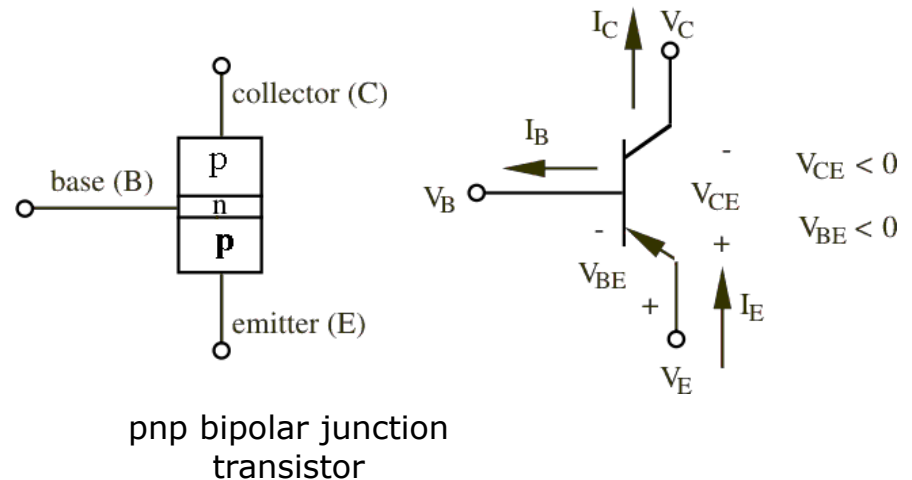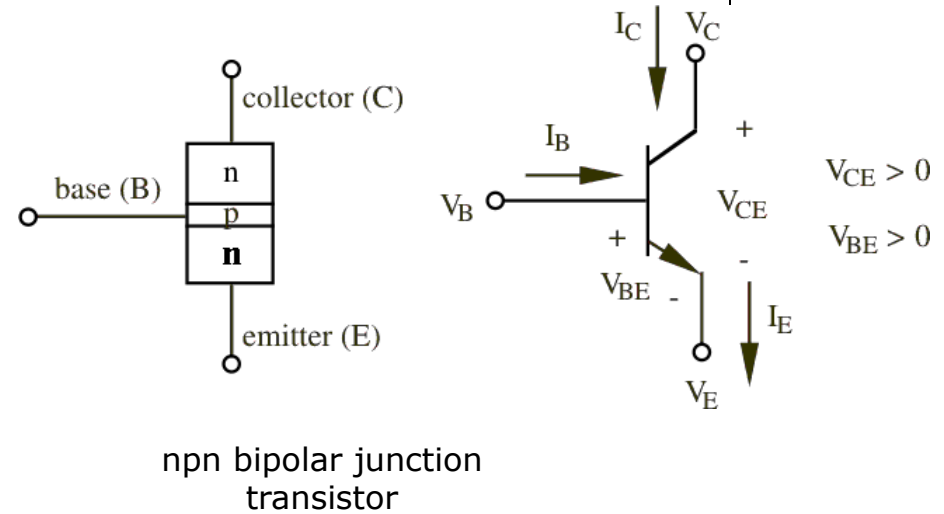- 3 adjacent regions of doped Si (each connected to a lead):
  - Base. (thin layer, less doped).
  - Collector.
  - Emitter.
- 2 types of BJT:
  - npn.
  - pnp.
- Most common: npn (focus on it).



Developed by  
Shockley  
(1949)





# BJT npn Transistor



- 1 thin layer of p-type, sandwiched between 2 layers of n-type.
- N-type of emitter: more heavily doped than collector.
- With  $V_C > V_B > V_E$ :
  - Base-Emitter junction forward biased, Base-Collector reverse biased.
  - Electrons diffuse from Emitter to Base (from n to p).
  - There's a depletion layer on the Base-Collector junction → no flow of e<sup>-</sup> allowed.
  - **BUT** the Base is thin and Emitter region is n<sup>+</sup> (heavily doped) → electrons have enough momentum to cross the Base into the Collector.
  - The small base current  $I_B$  controls a large current  $I_C$

$$V_C > V_B > V_E$$
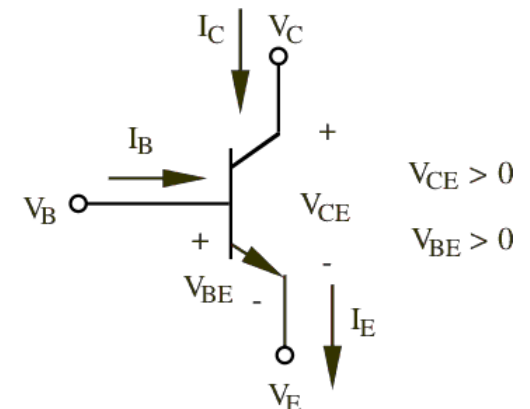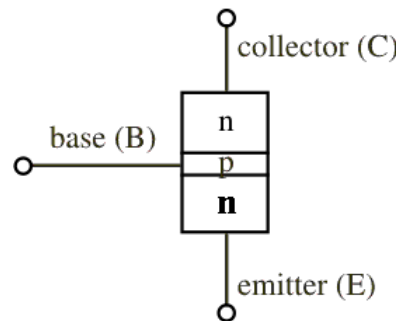
$$\begin{aligned}I_E &= I_C + I_B \\V_{BE} &= V_B - V_E \\V_{CE} &= V_C - V_E \\I_C &= \beta I_B\end{aligned}$$



# BJT characteristics




- Current Gain:
  - $\alpha$  is the fraction of electrons that diffuse across the narrow Base region
  - $1 - \alpha$  is the fraction of electrons that recombine with holes in the Base region to create base current
- The current Gain is expressed in terms of the  $\beta$  (beta) of the transistor (often called  $h_{fe}$  by manufacturers).
- $\beta$  (beta) is Temperature and Voltage dependent.
- It can vary a lot among transistors (common values for signal BJT: 20 - 200).

$$I_C = \alpha I_E$$



$$I_B = (1 - \alpha) I_E$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

# npn Common Emitter circuit

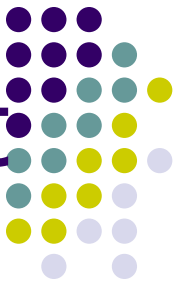

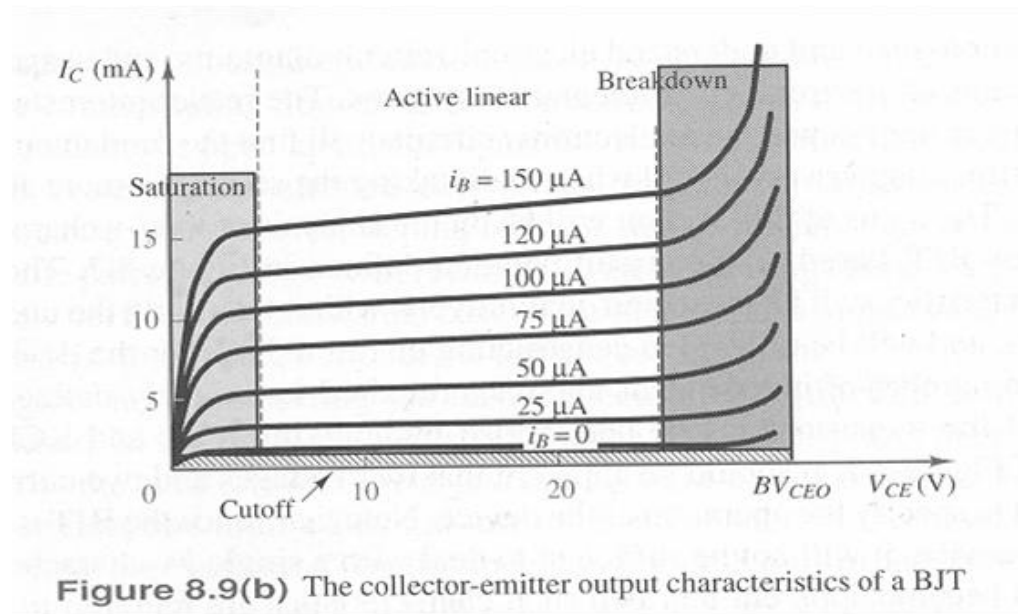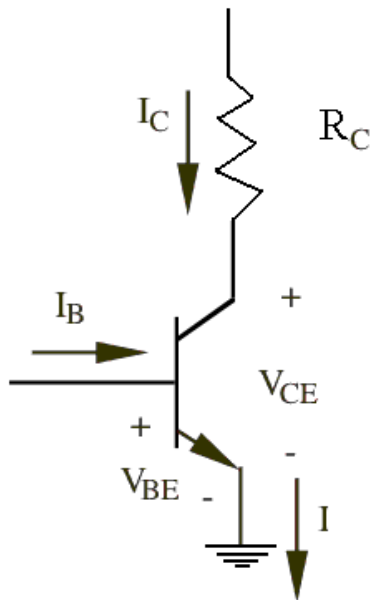- Emitter is grounded.
- Base-Emitter starts to conduct with  $V_{BE}=0.6V$ ,  $I_C$  flows and it's  $I_C=\beta \cdot I_B$ .
- Increasing  $I_B$ ,  $V_{BE}$  slowly increases to  $0.7V$  but  $I_C$  rises exponentially.
- As  $I_C$  rises, voltage drop across  $R_C$  increases and  $V_{CE}$  drops toward ground. (transistor in saturation, no more linear relation between  $I_C$  and  $I_B$ )



# Common Emitter characteristics



Collector current controlled by the collector circuit. ([Switch behavior](#))

In full saturation  $V_{CE}=0.2V$ .

No current flows

Collector current proportional to Base current

The avalanche multiplication of current through collector junction occurs: to be avoided


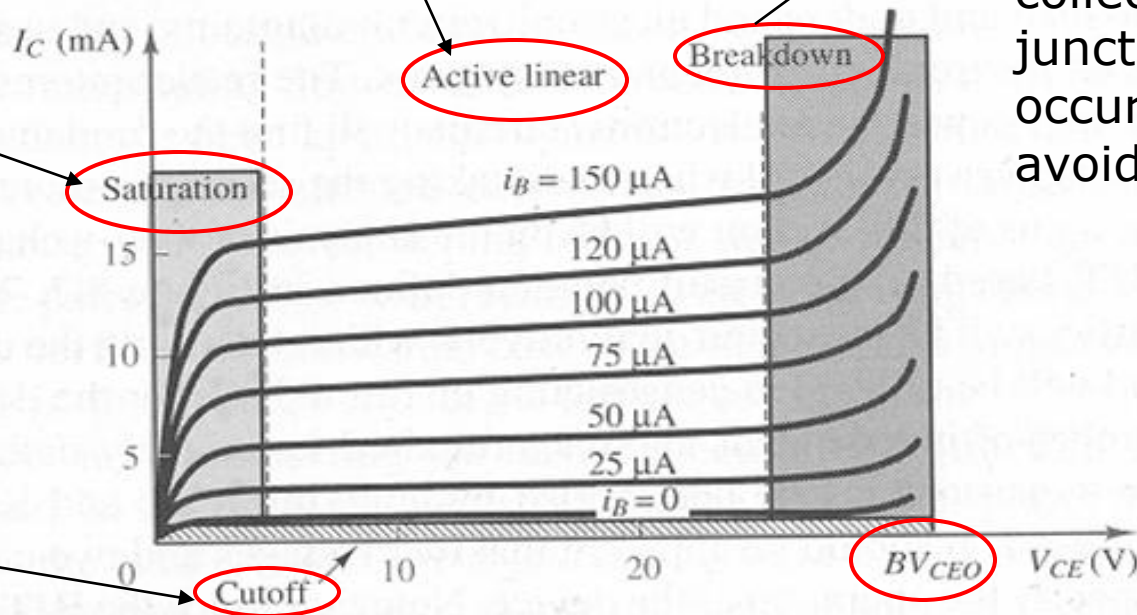



Figure 8.9(b) The collector-emitter output characteristics of a BJT

# BJT as Switch

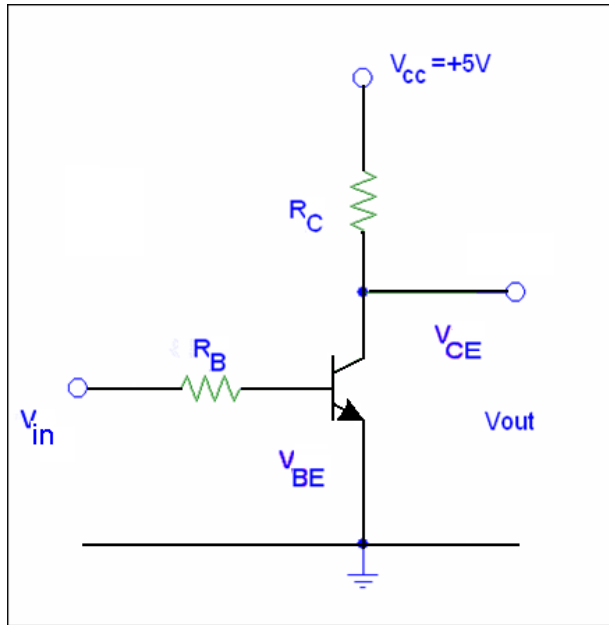

- $V_{in}(\text{Low}) < 0.7 \text{ V}$ 
  - BE junction not forward biased
  - Cutoff region
  - No current flows
  - $V_{out} = V_{CE} = V_{cc}$
- $V_{out} = \text{High}$

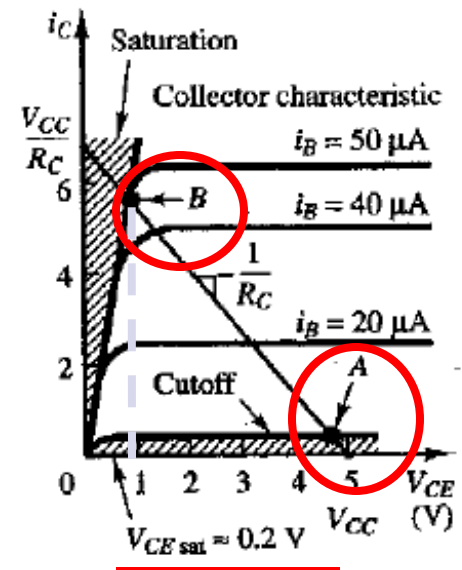- $V_{in}(\text{High})$ 
  - BE junction forward biased ( $V_{BE} = 0.7 \text{ V}$ )
  - Saturation region
  - $V_{CE}$  small ( $\sim 0.2 \text{ V}$  for saturated BJT)
  - $V_{out} = \text{small}$
  - $I_C = (V_{cc} - V_{CE}) / R_C$




# BJT as Switch 2




- Basis of digital logic circuits
- Input to transistor gate can be analog or digital
- Building blocks for TTL – Transistor Transistor Logic
- Guidelines for designing a transistor switch:
  - $V_C > V_B > V_E$
  - $V_{BE} = 0.7 \text{ V}$
  - $I_C$  independent from  $I_B$  (in saturation).
  - Min.  $I_B$  estimated from by ( $I_{Bmin} \approx I_C / \beta$ ).
  - Input resistance  $\rightarrow$  such that  $I_B > 5\text{-}10$  times  $I_{Bmin}$  because  $\beta$  varies among components, with temperature and voltage and  $R_B$  may change when current flows.
  - Calculate the max  $I_C$  and  $I_B$  not to overcome device specifications.

# BJT as Amplifier

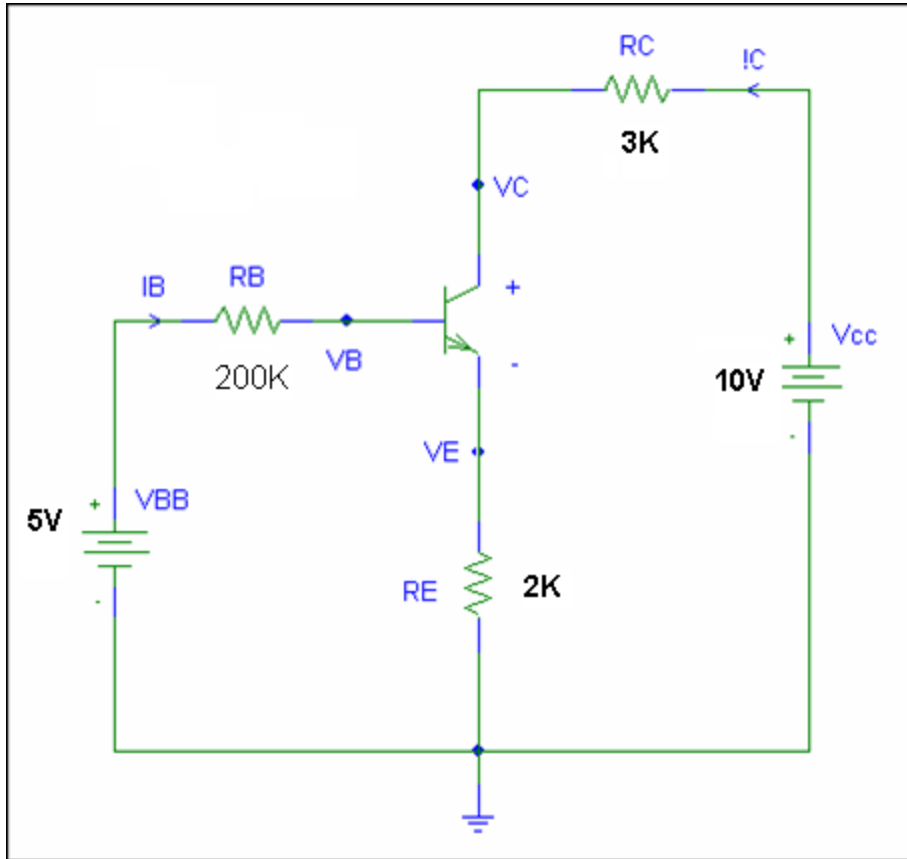

- Common emitter mode
- Linear Active Region
- Significant current Gain
- Example:
  - Let Gain,  $\beta = 100$
- Assume to be in active region ->  
 $V_{BE} = 0.7V$
- Find if it's in active region

# BJT as Amplifier

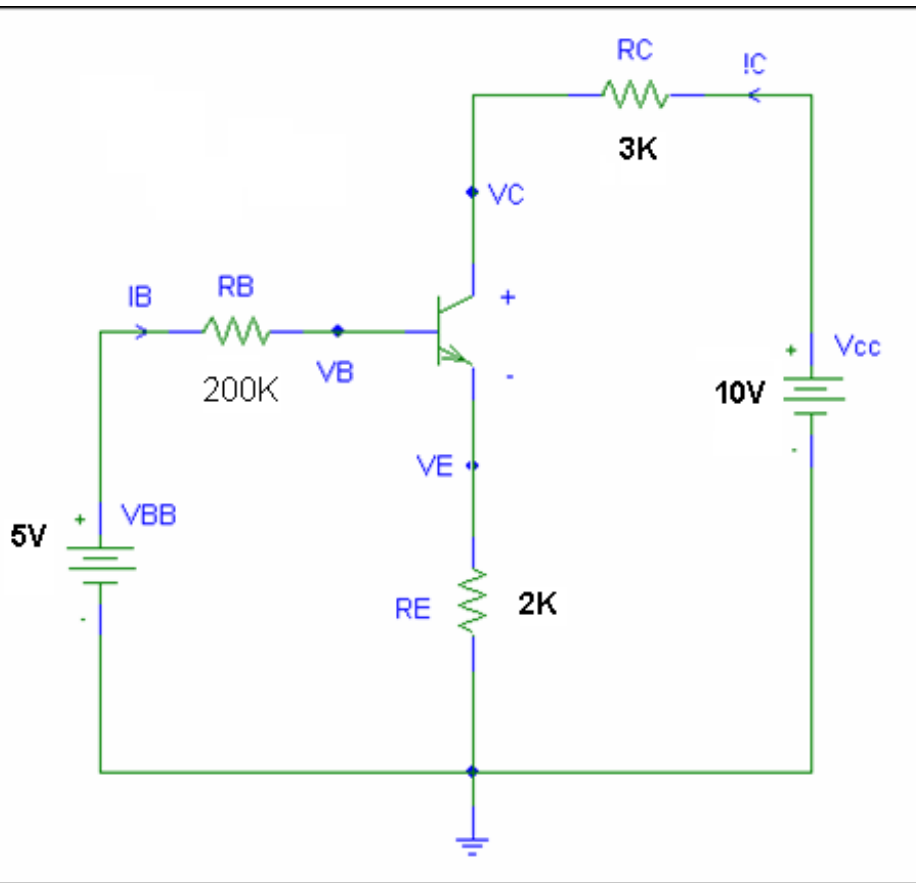

$$\underline{V_{BE}} = 0.7V$$

$$\underline{I_E} = I_B + I_C = (\beta + 1)I_B$$

$$\underline{I_B} = \frac{V_{BB} - V_{BE}}{R_B + R_E * 101} = \frac{5 - 0.7}{402} = 0.0107mA$$

$$\underline{I_C} = \beta * I_B = 100 * 0.0107 = 1.07mA$$

$$\begin{aligned} \underline{V_{CB}} &= V_{CC} - I_C * R_C - I_E * R_E - V_{BE} = \\ &= 10 - (3)(1.07) - (2)(101 * 0.0107) - 0.7 = \\ &= 3.93V \end{aligned}$$

$V_{CB} > 0$  so the BJT is in active region