

Department of Computer Engineering
University of Peradeniya

CO221 - Digital Design
Introduction to Verilog HDL


Exercise 1

Write a Verilog stimulus module which displays the message “Hello World!” and simulate it.

Exercise 2

A 4-bit parallel shift register has I/O pins as shown in the figure below. Write the module definition for this module `shift_reg`. Include the list of ports and port declarations. You do not need to show the internals.

Next, write a Declare a top-level module stimulus. Define `REG_IN` (4 bit) and `CLK` (1 bit) as reg register variables and `REG_OUT` (4 bit) as wire. Instantiate the module `shift_reg` and call it `sr1`.

 

Exercise 3


Create your own 2-input Verilog gates called `my-or`, `my-and` and `my-not` from 2-input nand gates. Check the functionality of these gates with a stimulus module.

Exercise 4

A 2-input xor gate can be built from `my_and`, `my_or` and `my_not` gates. Construct an xor module in Verilog that realizes the logic function, $z = xy' + x'y$. Inputs are `x` and `y`, and `z` is the output. Write a stimulus module that exercises all four combinations of `x` and `y` inputs.

Exercise 5

Build a 4 x 1 multiplexer using the logic circuit given below. Test the functionality of the circuit using a stimulus module.

 

Exercise 6

Build a 2 x 4 decoder using the logic circuit given below. Test the functionality of the circuit using a stimulus module.

